

# Electric Circuits

## Ohms Law

The amount of electric current through a metal conductor, at a constant temperature, in a circuit is proportional to the voltage across the conductor and can be described by:

$$I = V/R$$


where:

- $I$  = current through the conductor
- $V$  = voltage across the conductor
- $R$  = resistance of the conductor.


> The resistance of the conductor is constant, independent of the voltage applied across it or current passed through it.
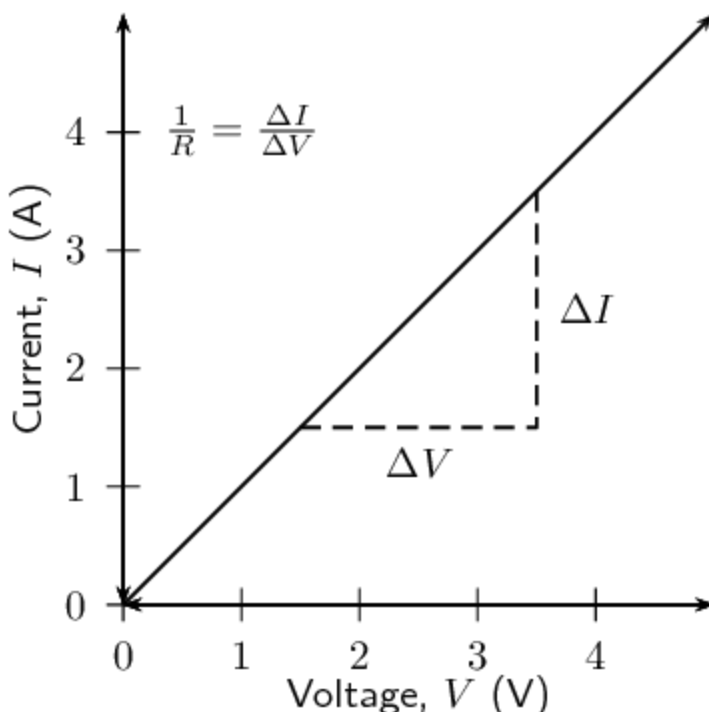
## Ohmic vs non-ohmic conductors



- Ohmic conductors obey ohms law: the graph of voltage against current is linear



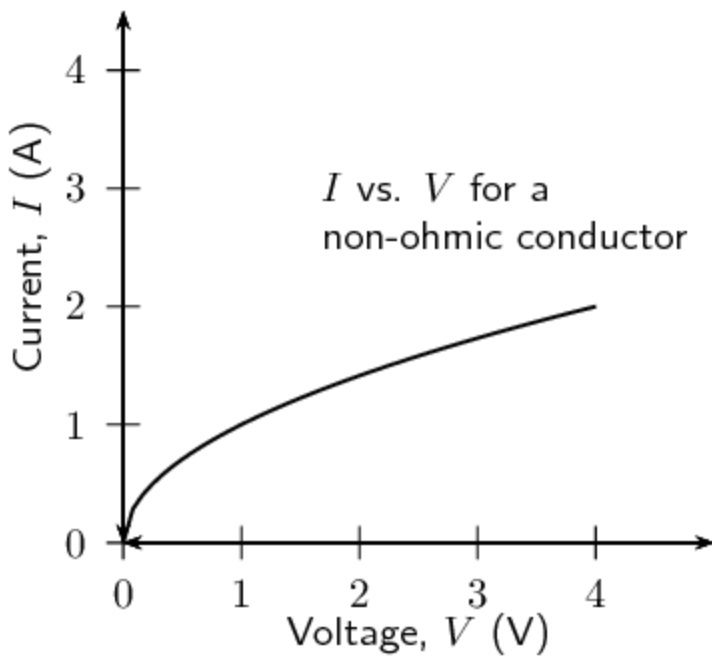- Non-Ohmic conductors do not obey ohms law therefore the graph of voltage against resistance is non-linear
- Mainly changes due to temperature changes



## Resistors in series and in parallel

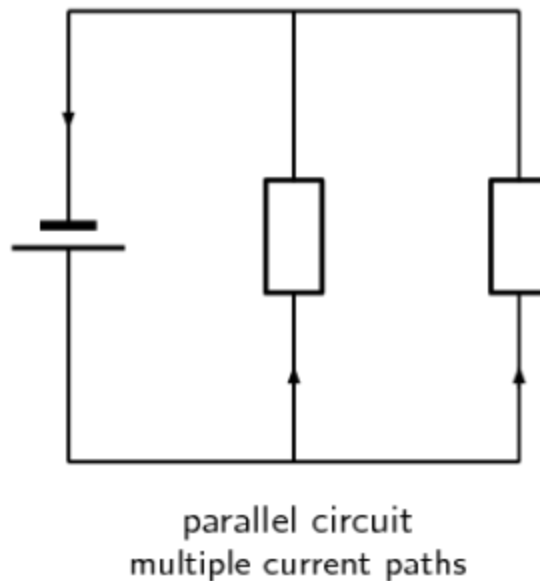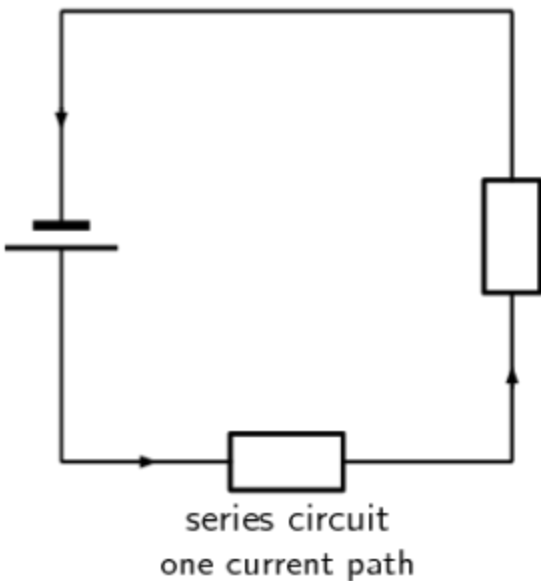

### Series circuit

$$R_s = R_1 + R_2 + R_3 + \dots + R_n$$

$$I = I_1 = I_2 = I_3$$

$$V_{total} = V_1 + V_2 + V_3$$

## Parrallel circuits

$$1/R_p = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_n$$

$$I_{total} = I_1 + I_2 + I_3$$

$$V = V_1 = V_2 = V_3$$

## Power and energy

### Electrical Power

Electrical power is the rate at which electrical energy is converted in an electric circuit. Described by:

$$P = I * V$$

Where:

- P = Power in watts (W)
- I = Current in Ampres (A)
- V = Voltage in volts (V)

### Electrical Power

Electrical energy is simply power times time described by:

$$E = P * t$$

Where:

- E = Energy in joules (J)
- P = Power in watts (W)
- t = Time in seconds (s)

| Physical Quantities | Unit name | Unit symbol |
|---------------------|-----------|-------------|
| Current (I)         | Amperes   | A           |

| Physical Quantities   | Unit name | Unit symbol |
|-----------------------|-----------|-------------|
| Electrical energy (E) | Joules    | J           |
| Power (P)             | Watts     | W           |
| Resistance (R)        | Ohms      | $\Omega$    |
| Voltage (V)           | Volts     | V           |